
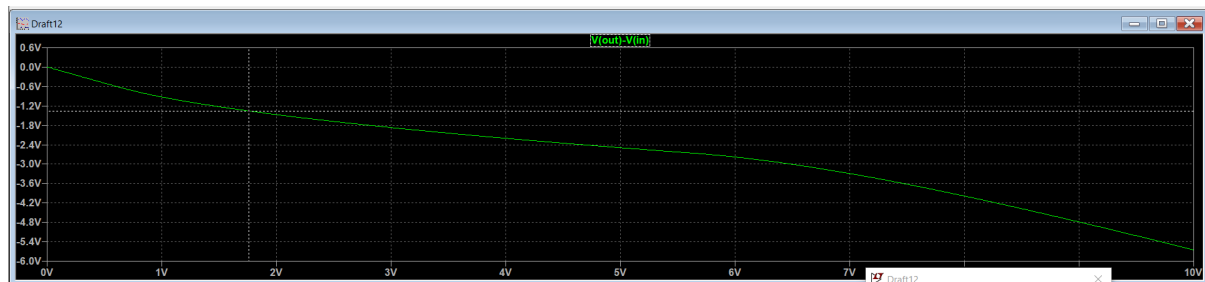


DC Voltage Shifter/Source Follower

1. When Resistor Load is there:

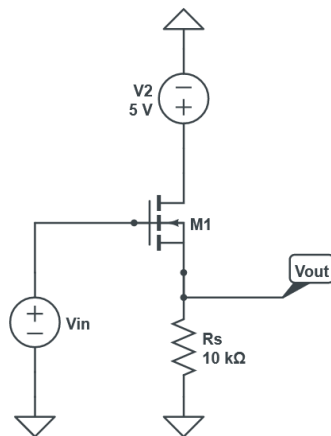


With Resistor load




- In this case output voltage V_{out} will depend on square-root of input voltage V_{in} .
- because current varies as function of input voltage due to finite resistance R_s .

2. Ideal Current Source

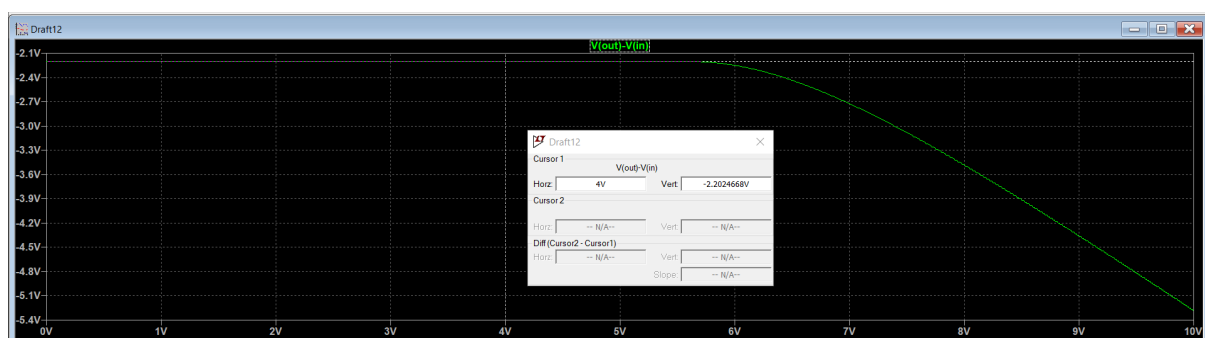


Ideal Current source

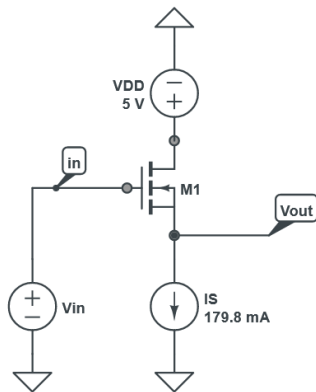- As this is ideal current source with infinite parallel resistance, $V_{out} - V_{in}$ remains constant till M1 is in saturation




3. MOSFET Current Source

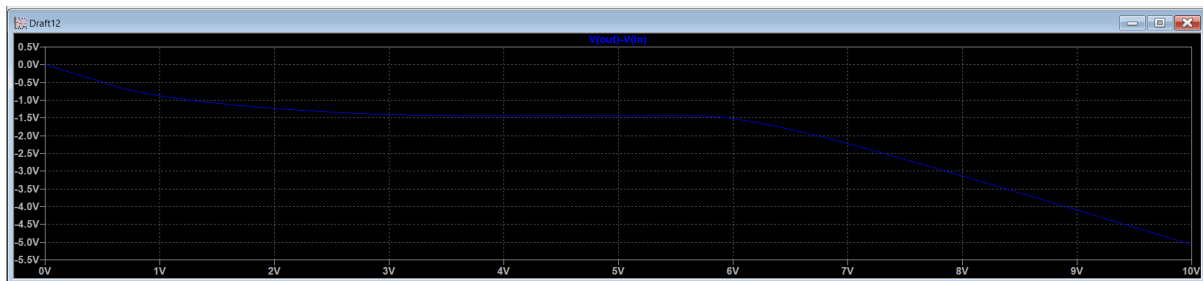

Current source using MOSFET

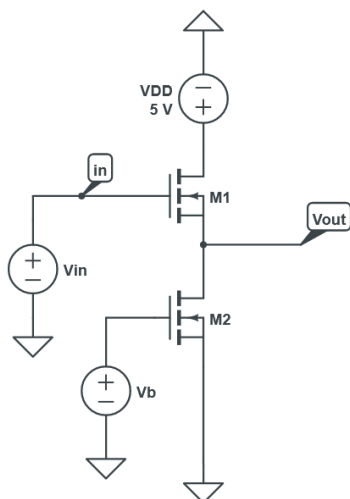- In this case there is finite r_o due to channel length modulation but, $V_{out} - V_{in}$ remains constant for some range of V_{in} .



<https://s3-us-west-2.amazonaws.com/secure.notion-static.com/04540a74-7a82-44e0-ab2a-e288dbdf19ab/Draft12.asc>