


# PROBLEM - 1

## Common Source Amplifier

Note:- → Model used in this problem contains non-linear effects, which are simulated in LTSpice.

→ Hence its parameters such as  $G_{m1}$ ,  $G_{m2}$ ,  $\frac{V}{L}$  are taken from results obtained in operating point simulation in LTSpice.
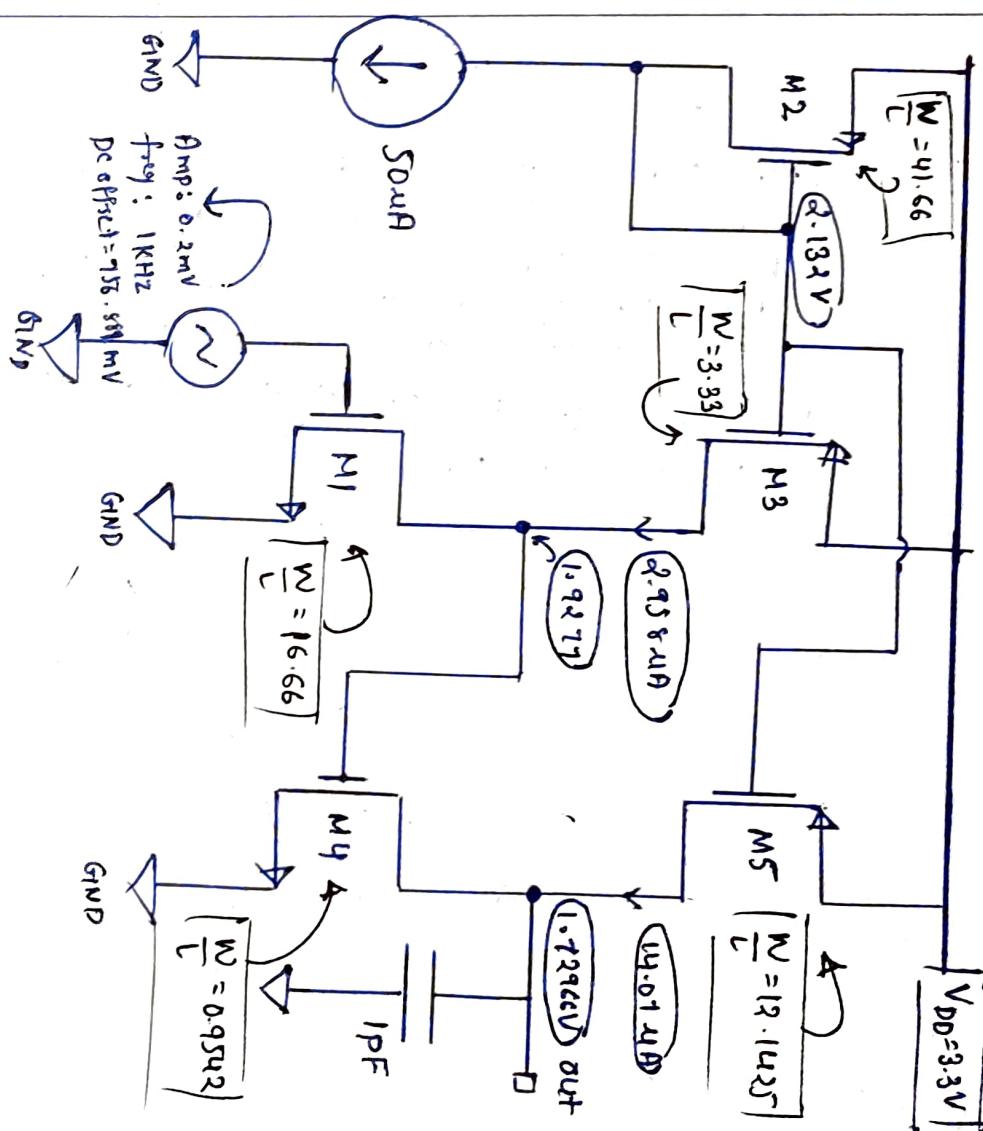
### \* Amplifier Configuration (Topology)



**Note:** We have used simulation to find all the  $(W/L)$ , for all MOSFETs because hand calculation may lead to wrong results because given model is non-linear and it contains effects other than channel length modulation and Body-bias effect.

### \* Method for finding $(W/L)$ of all the MOSFETs.

[1] First  $V_{DQ}$  of PMOS is  $0.927\text{ V}$ , and we want  $V_{DS}$  of  $0.2 - 0.3\text{ V}$  so we decided to keep  $V_{DS}$  of M2 around  $0.2 - 0.3\text{ V}$  so if  $V_{GS1}$  will be  $1.2\text{ V}$  so  $V_{G1} = 2.1\text{ V}$ , from this we simulated  $(W/L)$  by doing parameter sweep by keeping  $L = 2\text{ Lmin} = 1.2\mu\text{m}$ .

$$\rightarrow \text{we got } [W = 50\mu\text{m} \Rightarrow V_{G1} = 2.132\text{V}]$$

[2] Now we have chosen value by  $\frac{(W)}{L}$  of M3 by assuming some small current of  $5\mu\text{A}-10\mu\text{A}$ , and value of  $\frac{(W)}{L}$  of M1 by according to bias point like we need  $V_{DS} = 1.6\text{V}$  for a high output swing so for what given value of current we can get this  $V_{DS} \Rightarrow V_{G1S}$ .

**Note** By Applying Second-stage, we have changed the values again because to control gain and  $V_{DS}$ .

[3] Value of M5 is set for required gain, and value of M4 is ~~set~~ set such that it operates at  $V_{DS}$  (bias) of first stage, so no new voltage is required.

Q. (W) Values of  $M_3$  and  $M_5$  is chosen and tuned afterwards according to required gain (-70dB).

5. Here accurate hand calculations can't be done because  $V_{DS}$  of both the NMOS varieties is very sensitive to ( $\frac{W}{L}$ ) and bias points. That's how we can get such high gain.

→ So, at every point ( $\frac{W}{L}$ ) is simulated after but before that bias  $V_{GDS}$  is set for  $M_1$  from VTC of first stage and  $\frac{W}{L}$  of  $M_5$  is tuned for gain.

→ Now, we got ( $\frac{W}{L}$ ) of all the MOSFETs so we can generate small signal model of given amplifier.

⇒ Justification for all the MOSFETs are in active region:

$M_1$ : $V_{GSI} = 0.757V$	$M_2$ : $V_{GDS} = 1.11V$	$M_3$ : $V_{SBI} = 1.11V$
NMOS $V_{th} = 0.614V$ $V_{DS} = 1.93V$	PMOS $V_{SBI} = 1.11V$ $V_{SD} = 1.11V$ $V_{IN} = -0.926V$	PMOS $V_{SD} = 1.37V$ $V_{th} = -0.945V$

$M_4$ : $V_{GSI} = 1.93V$	$M_5$ : $V_{GDS} = 1.11V$
NMOS $V_{DS} = 1.93V$ $V_{th} = 1.15V$	$V_{SD} = 1.51V$ $V_{th} = -0.930V$

From the Simulation :-

$$M1 : g_m = \cancel{1.14 \times 10^4} \text{ A/V} \quad 6.54 \times 10^5 \text{ A/V}$$

$$g_{mb} = \cancel{8.86 \times 10^5} \text{ A/V} \quad 9.25 \times 10^5 \text{ A/V}$$

$$\tau_o = \cancel{1.087} \text{ n}\Omega \quad 3.5714 \text{ n}\Omega$$

$$M4 : g_m = 3.20 \times 10^5 \text{ A/V}$$

$$g_{mb} = 1.33 \times 10^5 \text{ A/V}$$

$$\tau_o = 0.4038 \text{ n}\Omega$$


$$M5 : \tau_o = 1.0869 \text{ n}\Omega$$

$$M3 : \tau_o = 4.7393 \text{ n}\Omega$$
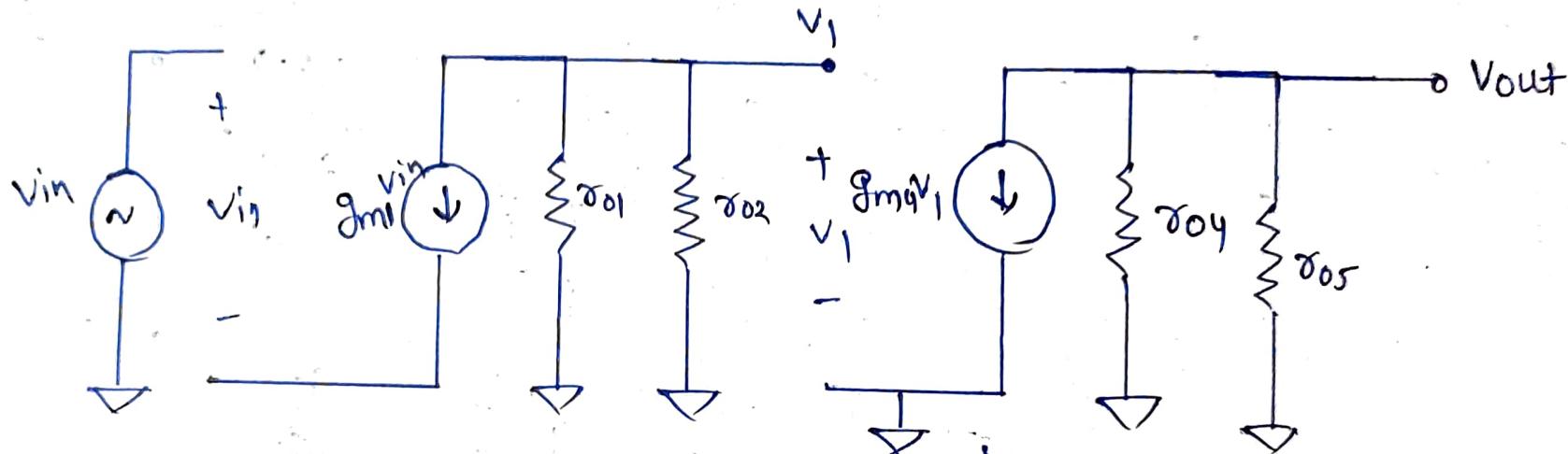
### \* Small Signal Model :-

Note :- This small signal is based on what is taught in class. It does not contain parasitic capacitance, input resistance of MOSFET, any non-linear effect other than channel length modulation.

→ Purpose of this model to estimate  
 $A_v \rightarrow \underline{G_{ms}}$ ,  $\underline{R_{out}}$ .



From stage-1,

$$v_1 = -g_{m1} (r_{o1} \parallel r_{o2}) \cdot v_{in}$$

from stage-2,

$$Vout = -g_{m2} (r_{o4} \parallel r_{o5}) \cdot v_1$$

from (1) and (2)


$$\frac{Vout}{V_{in}} = g_{m1} \cdot g_{m2} (r_{o1} \parallel r_{o2}) \cdot (r_{o4} \parallel r_{o5})$$

substituting values

$$\begin{aligned} \frac{Vout}{V_{in}} &= (6.54 \times 10^{-5}) (3.20 \times 10^{-5}) \\ &\quad \times (3.5714 \times 10^6 \parallel 4.7393 \times 10^6) \\ &\quad \times (1.0869 \times 10^6 \parallel 2.4038 \times 10^6) \\ &= 3190.2021 \end{aligned}$$

$$\frac{Vout}{V_{in}} = 3190.2021 \text{ dB} = \underline{\underline{170.07 \text{ dB}}}$$

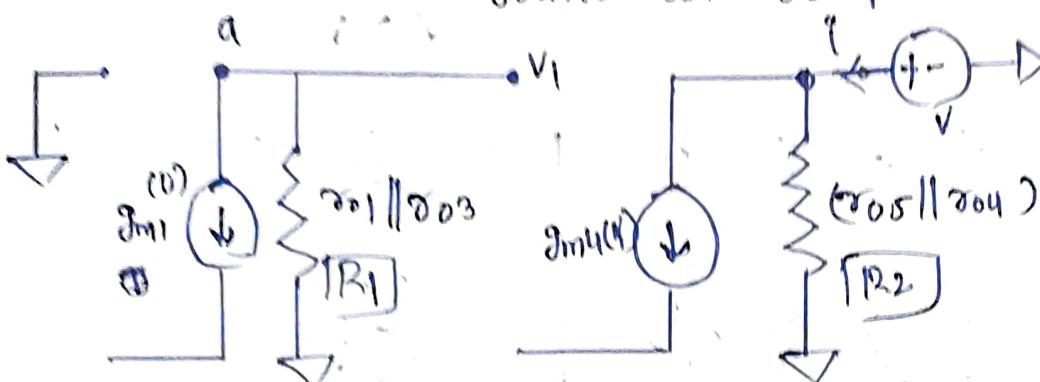$R_{out}$  can be calculated by switching off input source and applying voltage source at output node.



Current through first stage is zero because no voltage at input so current through  $R_1$  is also zero.

$$\Rightarrow \text{so } V_1 = 0 \times (\infty || \infty) \\ \boxed{V_1 = 0V}$$

Similarly current through  $R_2$  will be  $i$ .

$$\text{so } V = i (\infty || \infty)$$

$$\frac{V}{i} = \infty || \infty$$

$$R_{out} = \infty || \infty$$

In actual circuit there is one capacitor of  $1PF$ , so it will be added in ~~series~~ ~~parallel~~  $\infty$

$$(\infty || \infty) || \frac{1}{j\omega C}$$

$R_{out}$  =

= putting all values which gives

$$= 1.484 \times 10^5 \Omega = \boxed{0.1484 M\Omega}$$

## \* Specifications Review :-

### (1) Gain (Voltage)

Required  $\rightarrow$   $-10 \text{ dB}$

Obtained  $\rightarrow -10.011 \text{ dB}$

Reason  $\rightarrow$  Not required

### (2) $-3 \text{ dB}$ frequency

Required  $\rightarrow 3 \text{ kHz}$

Obtained  $\rightarrow 30 \text{ kHz}$

Reason  $\rightarrow$  Already better response than required.

### (3) Phase margin

Required  $\rightarrow 45^\circ$

Obtained  $\rightarrow \approx 0^\circ$

Reason  $\rightarrow$  we need to change value of load capacitance to change the phase margin otherwise, we will have to change Rout to shift the pole but this change will decrease gain so we have to trade-off between gain,  $3 \text{ dB}$  freq and phase margin

### (4) Power consumption

Required  $\rightarrow 3 \text{ mW}$

Obtained  $\rightarrow 114.47 \text{ uW}$

Reason  $\rightarrow$  already less than required, so no need.

### (5) Output swing

Required  $\rightarrow 4.64 \text{ V}$

Obtained  $\rightarrow 2.3 \text{ V}$

Reason  $\rightarrow$  little bit less due to because, we implemented Q-stepper and bias ( $V_{QSS}$ ) of second stage is much higher so  $V_{DD}$  is also much higher so output swing is limited at positive-puot.

$\rightarrow V_{DS} \geq V_{OV} \Rightarrow V_{DS} \geq V_{GDS} - V_{th}$

if  $V_{GDS} \uparrow \Rightarrow V_{DS} \uparrow$   
 so swing will be limited  
 at negative part.

### (6) Input Swing

Obtained  $\rightarrow 0.57mV$

### \* Small Signal Parameters of all the MOSFETs

M1

NMOS

$$g_m = 6.54 \times 10^5 \text{ A/V}$$

$$g_{mb} = 2.25 \times 10^5 \text{ A/V}$$

$$\gamma_0 = 3.5714 \times 10^{-6} \Omega$$

$$= 3.57 \text{ M}\Omega$$

M2

PMOS

$$g_m = 4.02 \times 10^4 \text{ A/V}$$

$$g_{mb} = 1.18 \times 10^4 \text{ A/V}$$

$$\gamma_0 = 0.265 \text{ M}\Omega$$

M3

PMOS

$$g_m = 2.58 \times 10^5 \text{ A/V}$$

~~$g_{mb} = 1.14 \times 10^4$~~ 

$$g_{mb} = 9.64 \times 10^{-6} \text{ A/V}$$

$$\gamma_0 = 4.7393 \text{ M}\Omega$$

M4

NMOS

$$g_m = 3.20 \times 10^5 \text{ A/V}$$

$$g_{mb} = 1.33 \times 10^5 \text{ A/V}$$

$$\gamma_0 = 2.403 \text{ M}\Omega$$

M5

PMOS


$$g_m = 1.14 \times 10^4 \text{ A/V}$$



$$g_{mb} = 3.36 \times 10^5 \text{ A/V}$$

$$\gamma_0 = 1.0869 \text{ M}\Omega$$

$V_{out})/V_{(in)}$

2019 A3 PS0158P | 2019 A3 PS0200P

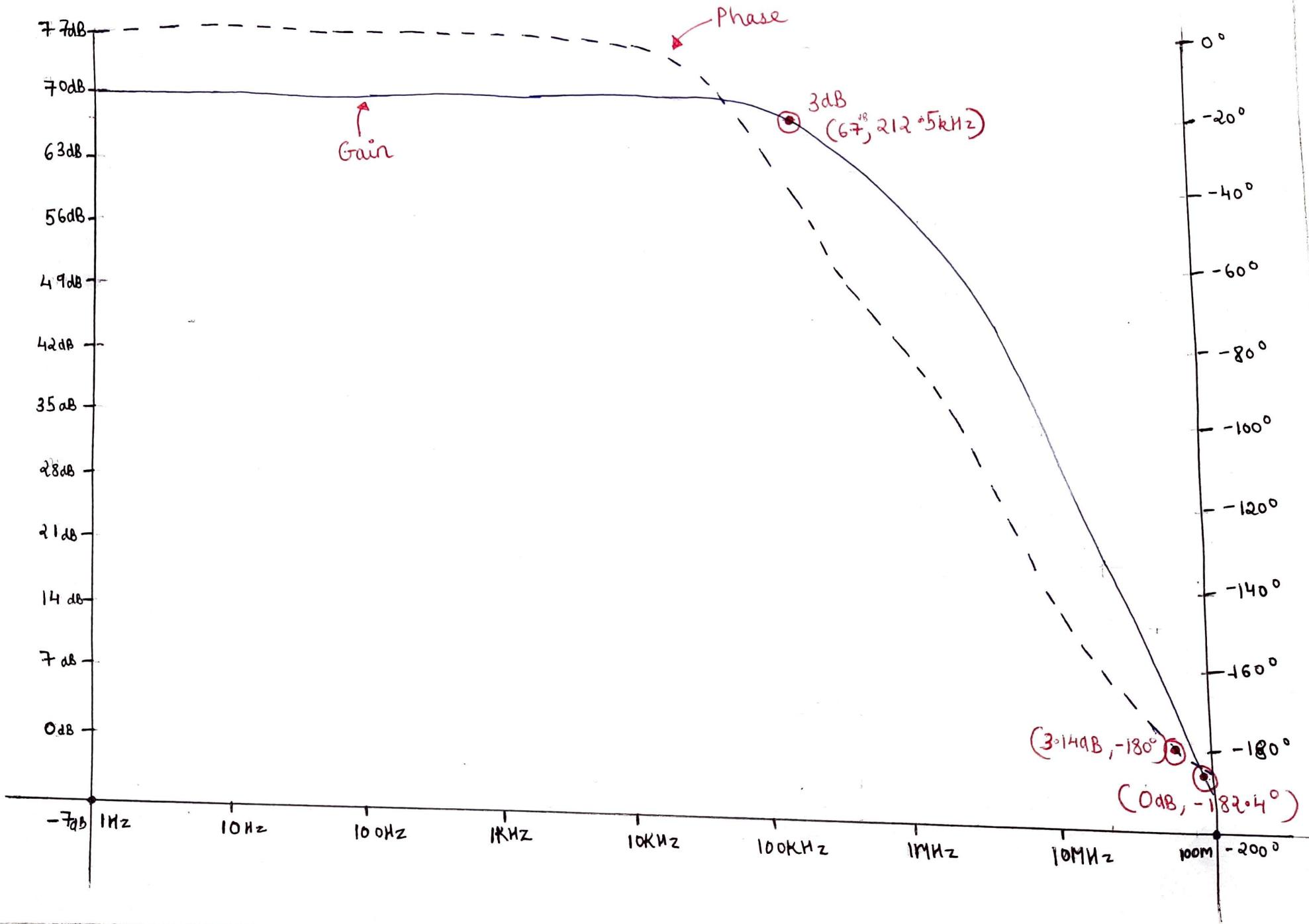

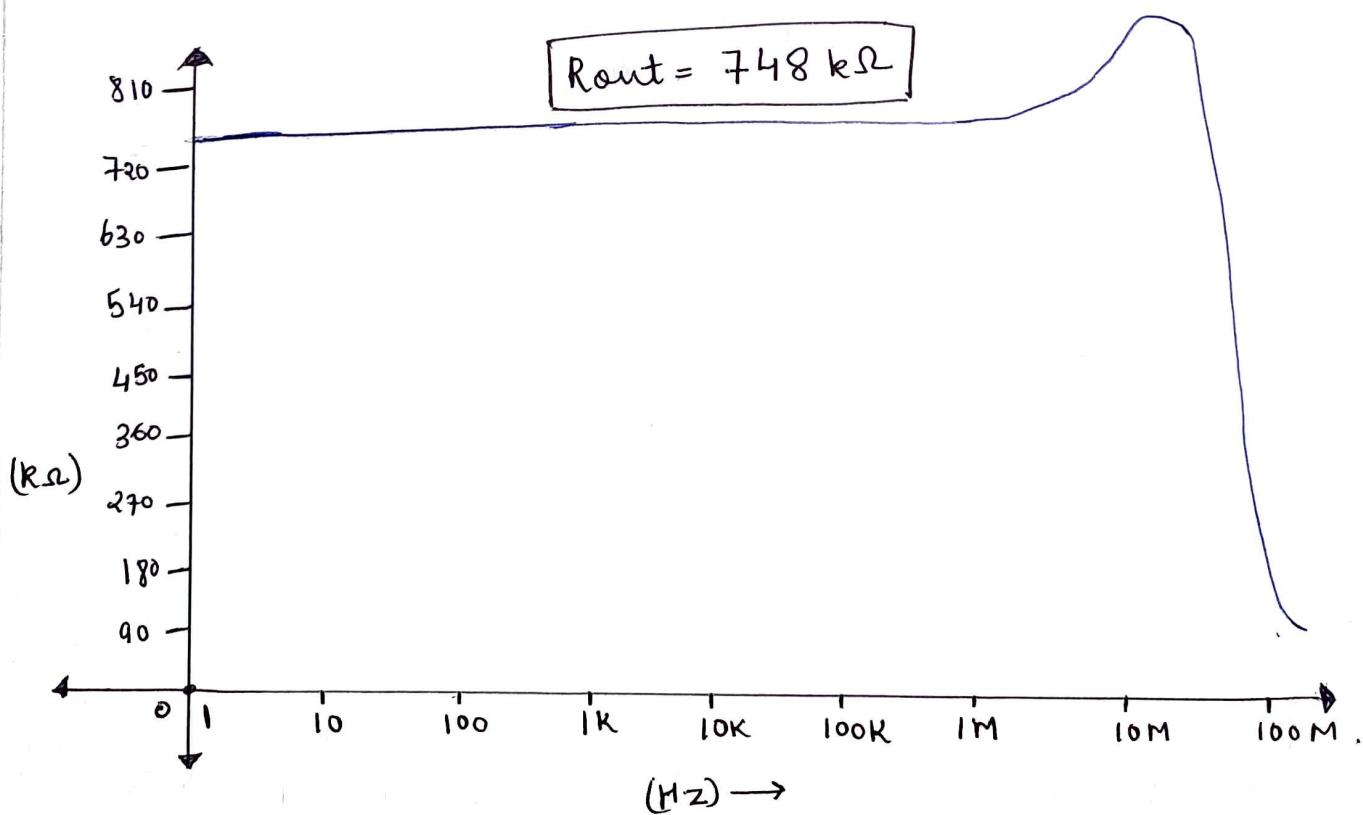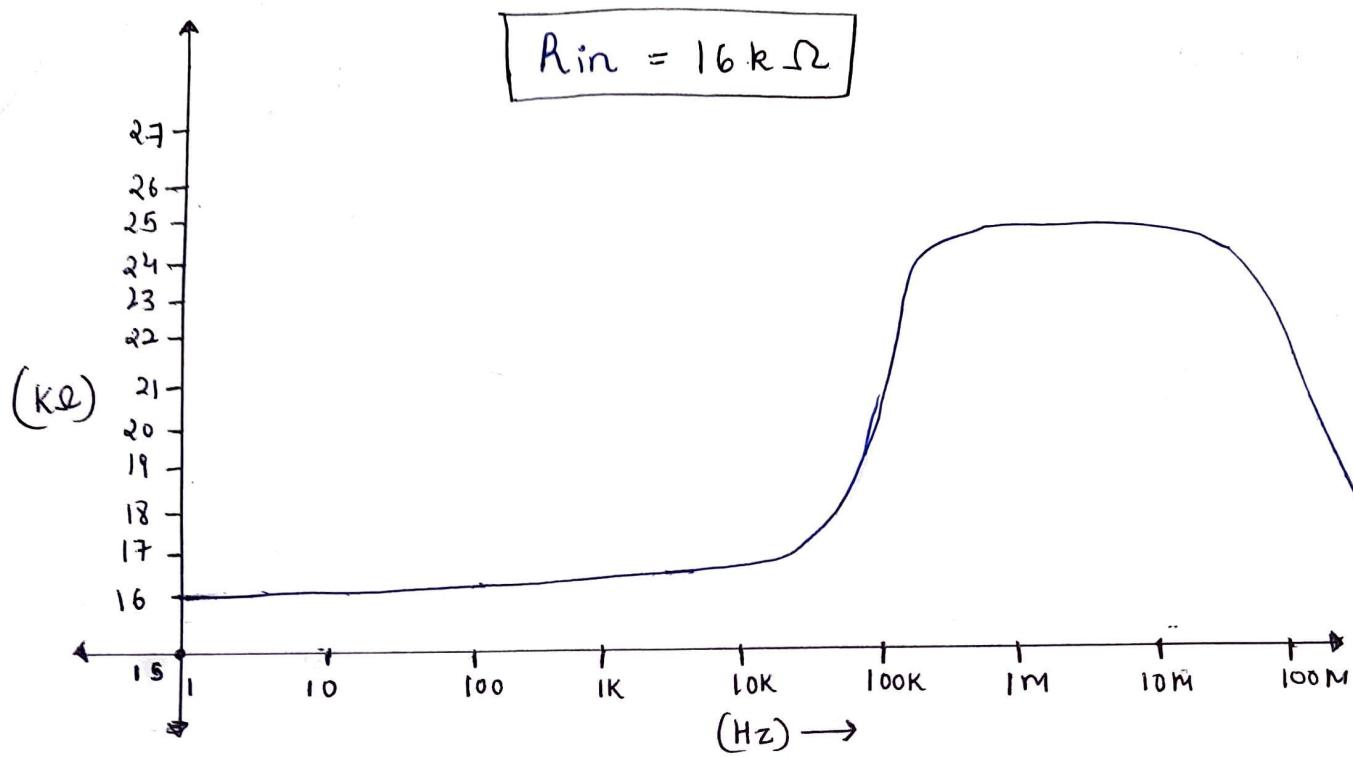

# Problem-1

## Code

```
* C:\Users\devan\Documents\assnmnt files(2)\final_1 - Copy.asc
M1 n2 in 0 0 NMOS l=1.2u w=20u
V1 in 0 SINE(756.88179m .2m 1k) AC 1
I1 n1 0 50μ
M2 n1 n1 N001 N001 PMOS l=1.2u w=50u
M3 n2 n1 N001 N001 PMOS l=1.2u w=4u
V2 N001 0 3.3
M4 out n2 0 0 NMOS l=1.2u w=1.145u
M5 out n1 N001 N001 PMOS l=1.2u w=14.571u
C1 out 0 7.2p
.model NMOS NMOS
.model PMOS PMOS
.lib C:\Users\devan\Documents\LTspiceXVII\lib\cmp\standard.mos
.op
;dc v1 0 5 0.0001
;tran 1
.opt plotwinspace=0
.include mue1.txt
;step param W 1.14u 1.15u 0.001u
;ac dec 1000 1 100Meg
.backanno
.end
```

## Error Log

```
Direct Newton iteration for .op point succeeded.
Semiconductor Device Operating Points:
      --- BSIM3 MOSFETS ---
      Name:      m5        m3        m2        m4        m1
Model:      pmos       pmos       pmos       nmos       nmos
Id:      -1.41e-05   -2.96e-06   -5.00e-05   1.41e-05   2.96e-06
Vgs:      -1.17e+00   -1.17e+00   -1.17e+00   1.93e+00   7.57e-01
Vds:      -1.57e+00   -1.37e+00   -1.17e+00   1.73e+00   1.93e+00
Vbs:      0.00e+00    0.00e+00    0.00e+00    0.00e+00    0.00e+00
Vth:      -9.30e-01   -9.45e-01   -9.26e-01   1.15e+00   6.74e-01
Vdsat:    -2.22e-01   -2.08e-01   -2.27e-01   4.87e-01   6.74e-02
Gm:       1.14e-04    2.58e-05    4.02e-04    3.20e-05    6.54e-05
Gds:      9.20e-07    2.11e-07    3.77e-06    4.16e-07    2.80e-07
Gmb:      3.36e-05    7.64e-06    1.18e-04    1.33e-05    2.25e-05
Cbd:      0.00e+00    0.00e+00    0.00e+00    0.00e+00    0.00e+00
Cbs:      0.00e+00    0.00e+00    0.00e+00    0.00e+00    0.00e+00
Cgsov:    4.06e-15    9.95e-16    1.43e-14    1.30e-16    3.90e-15
Cgdov:    4.06e-15    9.95e-16    1.43e-14    1.30e-16    3.90e-15
```

Cgbov:	1.09e-15	1.09e-15	1.09e-15	1.13e-15	1.13e-15
dQgdVgb:	3.88e-14	1.04e-14	1.34e-13	2.87e-15	4.98e-14
dQgdVdb:	-4.06e-15	-9.96e-16	-1.43e-14	-1.28e-16	-3.84e-15
dQgdVsb:	-3.14e-14	-7.73e-15	-1.11e-13	-1.52e-15	-3.61e-14
dQddVgb:	-1.67e-14	-4.08e-15	-5.89e-14	-7.38e-16	-2.03e-14
dQddVdb:	4.06e-15	9.96e-16	1.43e-14	1.29e-16	3.86e-15
dQddVsb:	1.65e-14	4.04e-15	5.82e-14	8.84e-16	2.24e-14
dQbdVgb:	-5.49e-15	-2.19e-15	-1.64e-14	-1.40e-15	-9.08e-15
dQbdVdb:	-4.24e-19	-1.64e-19	-4.71e-18	5.87e-19	2.24e-17
dQbdVsb:	-5.61e-15	-1.35e-15	-2.00e-14	-3.79e-16	-1.26e-14


Date: Sun Apr 11 17:45:44 2021  
 Total elapsed time: 0.097 seconds.

```

tnom = 27
temp = 27
method = trap
totiter = 13
traniter = 0
tranpoints = 0
accept = 0
rejected = 0
matrix size = 7
fillins = 0
solver = Normal
Matrix Compiler1: 312 bytes object code size
Matrix Compiler2: 555 bytes object code size
  
```

## PROBLEM- 2

Emitter    follower

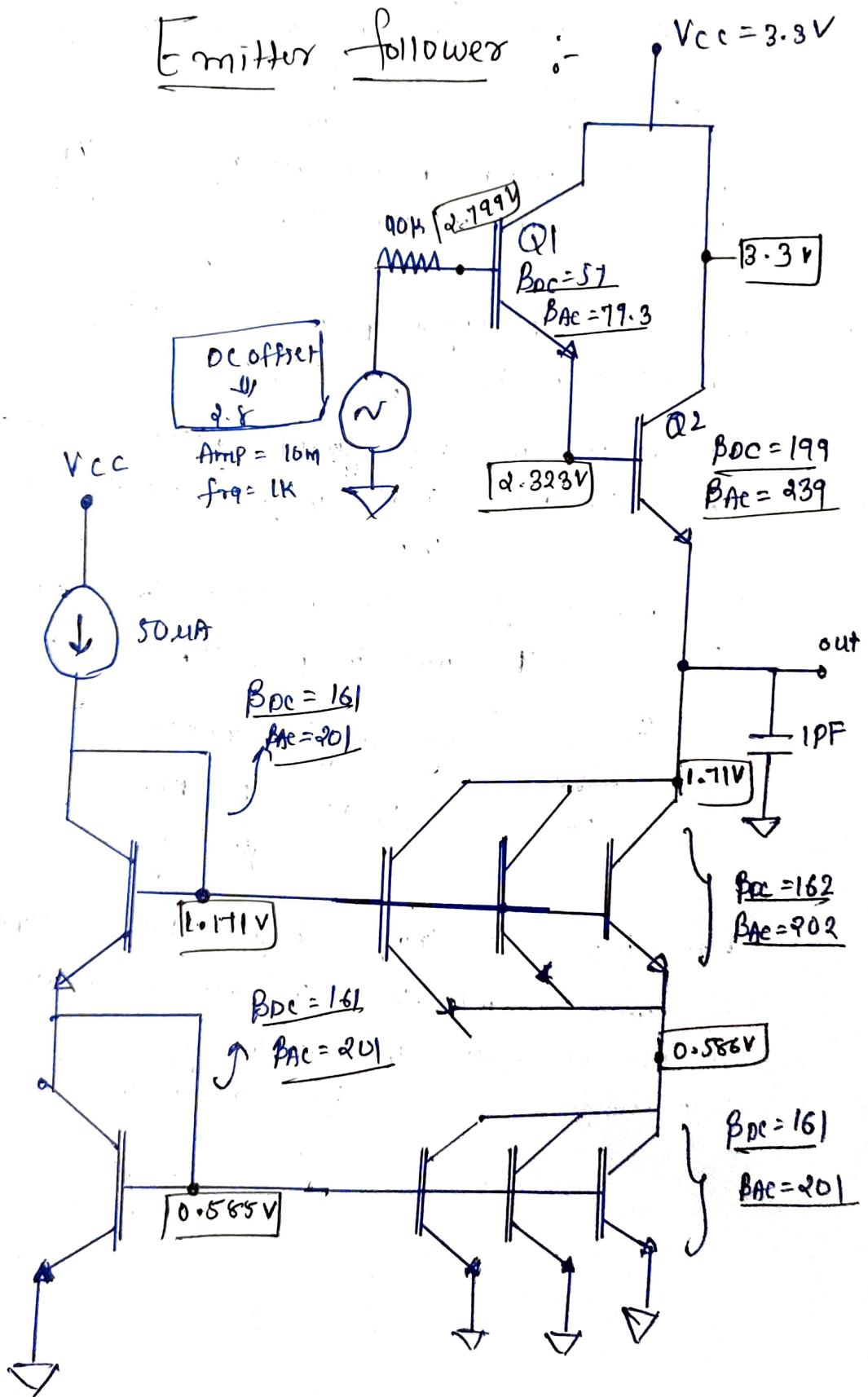

## \* Design Methodology:


Note:- Here in case of BJTs, we can only change  $I_c$  to control  $g_m$  and  $r_{ff}$  because of

$$g_m = \frac{I_c}{V_t} \quad , \quad r_{ff} = \frac{\beta}{g_m}$$

So, to obtain proper biasing multiple BJTs are used in parallel.

- [1] we used Darlington pair to amplify current gain by larger factor;
- [2] After which we have used Active cascode load to get  $\frac{r_{out}}{V_{in}}$  very close to unity.
- [3] To increase  $g_m$   $I_c$  should be increased so 3 BJTs used in parallel, so net  $I_c = \frac{3 I_{REF}}{1 + \frac{B_A C}{\beta}}$ , by using expression  $I_{net} = \frac{N \cdot I_{REF}}{1 + \frac{C(N+1)}{\beta}}$
- [4] but here one thing should be kept in mind that  $r_{ff}$  decreases as ~~increases~~ with increase in  $g_m$  so current gain might decrease by further increase in  $I_c$ .

\* Small Signal model :-

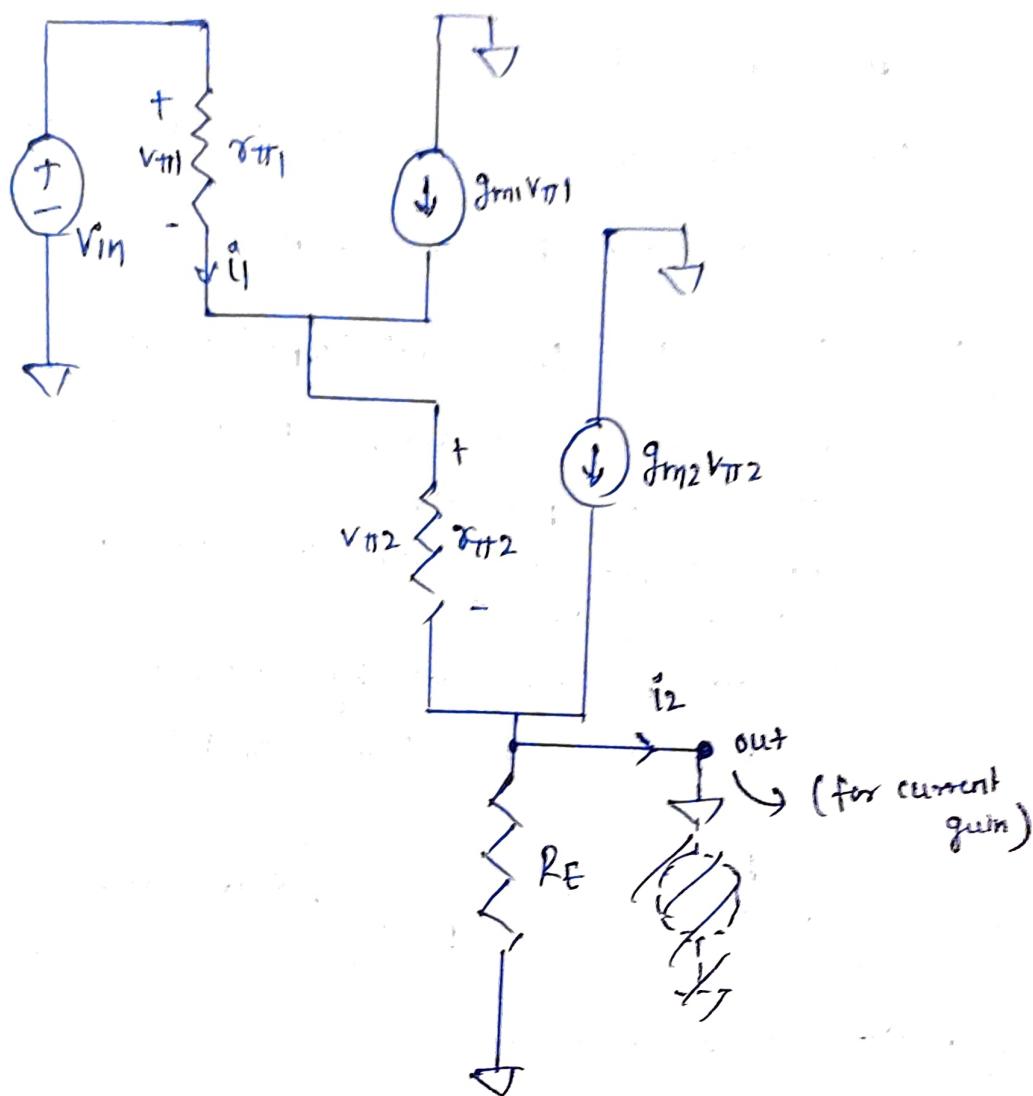

\* Current gain :-

$i_2$  can be simply calculated by following

method

$$i_2 = i_1 (\beta_1 + 1) (\beta_2 + 1) \quad , \quad \beta_1 > \beta_2 \rightarrow \text{AC current gains.}$$

$$\tilde{\beta}_1 = \frac{(\beta_1 + 1)(\beta_2 + 1)}{\text{by putting values}}$$

$$\tilde{\beta}_1 = \frac{19120}{85.48 \text{ dB}}$$

And note that

$$\tilde{\beta}_1 (\text{simulated}) = 85.652 \text{ dB}$$

$$R_{out} = R_E \parallel \left[ (\gamma_{e2} + \frac{r_{e1} + [R_{sig} \parallel (B_2+1)]}{B_2+1}) \right]$$

Here note that,

$R_E$  → active ~~load~~ load of emitter degeneration.

it can be calculated by this expression.

$$R_E = (\gamma_{05/3}) + (g_{ms} \cdot r_{05} + 1) (\gamma_{05} \parallel (\gamma_{06/3}))$$

→ here we used  $\gamma_{05/3}$  because 3 BJTs are in parallel.

→ And  $g_{ms}$  is used for equivalent current gain.

→ It can be understood by assuming 3 BJTs as  $\frac{\text{one}}{3} (3g_m, \frac{r_0}{3})$  BJT.

$$\gamma_{e2} = \frac{\gamma_{05/2}}{B_2+1}, \quad \gamma_{e1} = \frac{\gamma_{01}}{B_1+1}, \quad R_{sig} = 40\text{k}\Omega$$

putting all the values,

$$R_{out} = 341.4577 \Omega$$

while,  $R_{out}(\text{simulated}) = 335 \Omega$ , which is quite close to hand-calculated.

$R_{in}$  can be calculated by following expression

$$R_{in} = R_{sig} + (\beta_1 + 1) [r_{e1} + (\beta_2 + 1)(r_{e2} + R_E)]$$

Putting all the values,  
we get

$$R_{in} = \cancel{5.56 \text{ M}\Omega} \cdot 3.8 \times 10^9 \Omega =$$

while calculated  $R_{in} = 3.6 \times 10^9 \Omega$   
simulated

### \* Specification Review :-

#### ① Current gain :-

Required  $\rightarrow 85 \text{ dB}$

Obtained  $\rightarrow 85.41 \text{ dB}$

Justification  $\rightarrow$  not required

#### ② -3dB frequency :-

Required  $\rightarrow 50 \text{ kHz}$

Obtained  $\rightarrow 2.322 \text{ kHz}$

Justification  $\rightarrow$  Because of ~~internal~~ ~~BJT~~  
internal capacitance of BJT is too high  
so pole is shifted left, and note that  
current gain ~~of~~ will not depend on  
load capacitance because of we are  
grounding output terminal. ~~and~~

Q.1 Output swing

Required  $\rightarrow 2.64V$   
 Obtained  $\rightarrow 1.98V (0.717 - 2.64)$

Justification  $\rightarrow$  Because we used darlington pair, that's why output swing will be limited by  $V_{CE} (V_{CE1} + V_{BE2})$  in upper bound which is approx. 2.64 V and we have used Cascaded load so there also ~~so~~ swing is limited by  $V_{BE1} + V_{CE}$  in lower bound, so much higher part of  $V_{CE}$  is used in keeping all BJTs in active region.

Q.2 Phase Margin

Required  $\rightarrow 115^\circ$   
 Obtained  $\rightarrow 126.168^\circ$

Justification  $\rightarrow$  much better than required, but one thing must be noted that this configuration has high phase margin and low 3dB frequency while in problem-1 configuration, which had higher 3dB frequency and lower phase margin, in that we can control by load capacitance but in this case we can not.

Q.3 Power Dissipation

Required  $\rightarrow 3mW$   
 Obtained  $\rightarrow 501.6 \mu W$

Justification  $\rightarrow$  much less than required, so better performance.

## \* Small Signal Parameters of all BJTs

$\alpha_1$  (NPN)

$$g_m = 2.71 \times 10^{-5} \text{ A/A}$$

$$\gamma_{ff} R_{ff} = 4.92 \text{ M}\Omega$$

$$\gamma_0 = 8.56 \times 10^7 \Omega$$

$$= 85.6 \text{ M}\Omega$$

$$\beta_{DC} = 54 \quad \beta_{AC} = 19.3$$

$\alpha_2$  (NPN)

$$g_m = 5.49 \times 10^{-3} \text{ A/A}$$

$$\gamma_{ff} = 4.34 \times 10^4 \Omega$$

$$\gamma_0 = 1.26 \times 10^5 \Omega$$

$$\beta_{DC} = 199$$

$$\beta_{AC} = 239$$

$\alpha_3$  (NPN) NPN

$$g_m = 1.89 \times 10^{-3} \text{ A/A}$$

$$\gamma_{ff} = 1.07 \times 10^5 \Omega$$

$$\gamma_0 = 1.22 \times 10^6 \Omega$$

$$\beta_{DC} = 161$$

$$\beta_{AC} = 201$$

$\alpha_4$  (NPN) NPN

$$g_m = 1.85 \times 10^{-3} \text{ A/A}$$

$$\gamma_{ff} = 1.07 \times 10^5 \Omega$$

$$\gamma_0 = 1.24 \times 10^6 \Omega$$

$$\beta_{DC} = 161$$

$$\beta_{AC} = 201$$

$\alpha_5$ ,  $\alpha_9$ ,  $\alpha_{11}$

(NPN)

$$g_m = 1.84 \times 10^{-3} \text{ A/A}$$

$$\gamma_{ff} = 1.10 \times 10^5 \Omega$$

$$\gamma_0 = 1.26 \times 10^6 \Omega$$

$$\beta_{DC} = 1.62 \times 10^2 \quad 162$$

$$\beta_{AC} = 202$$

$\alpha_6$ ,  $\alpha_{10}$ ,  $\alpha_{12}$

(NPN)

$$g_m = 1.85 \times 10^{-3} \text{ A/A}$$


$$\gamma_{ff} = 1.08 \times 10^5 \Omega$$



$$\gamma_0 = 1.24 \times 10^6 \Omega$$

$$\beta_{DC} = 161$$

$$\beta_{AC} = 201$$

\* AC analysis

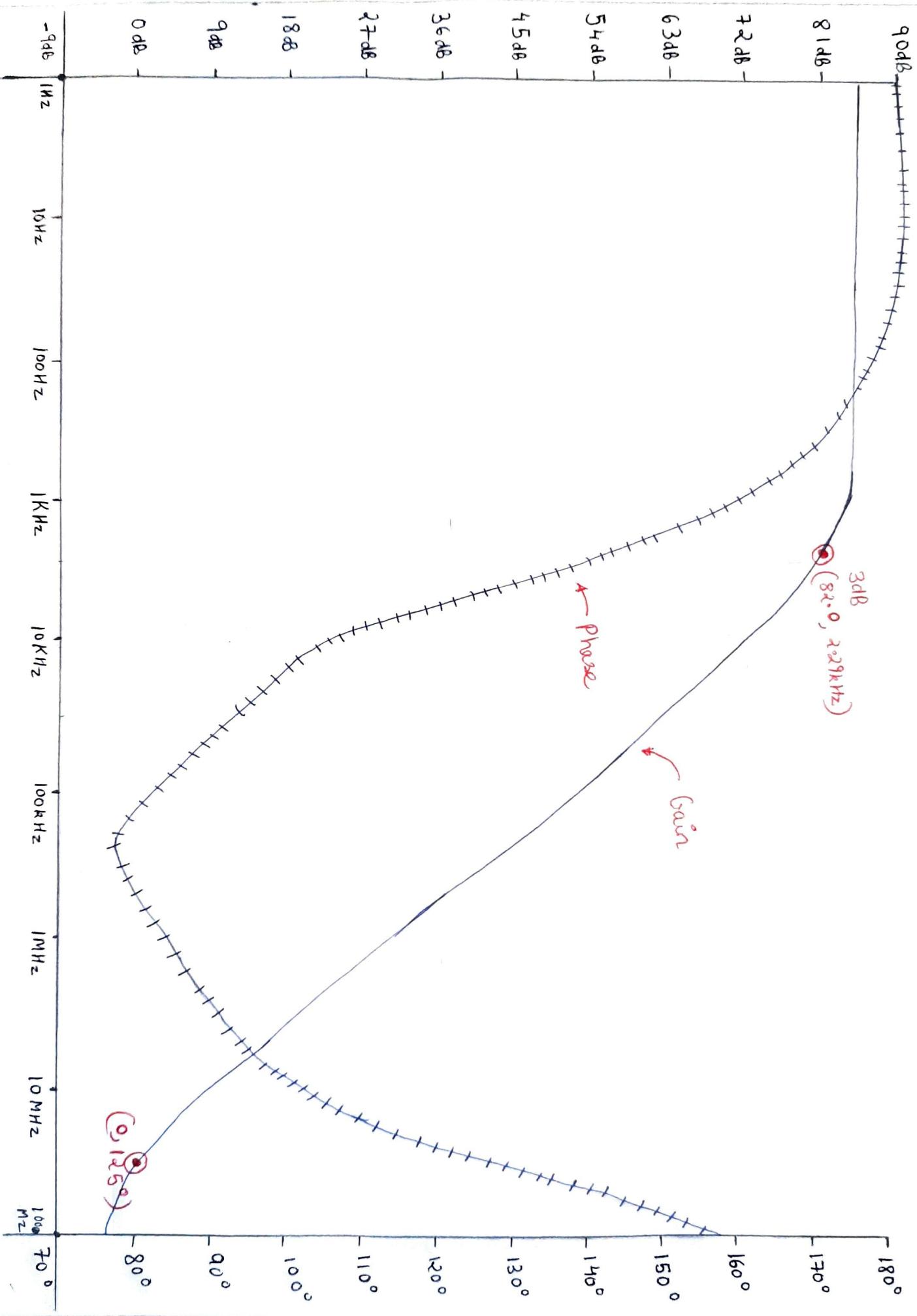

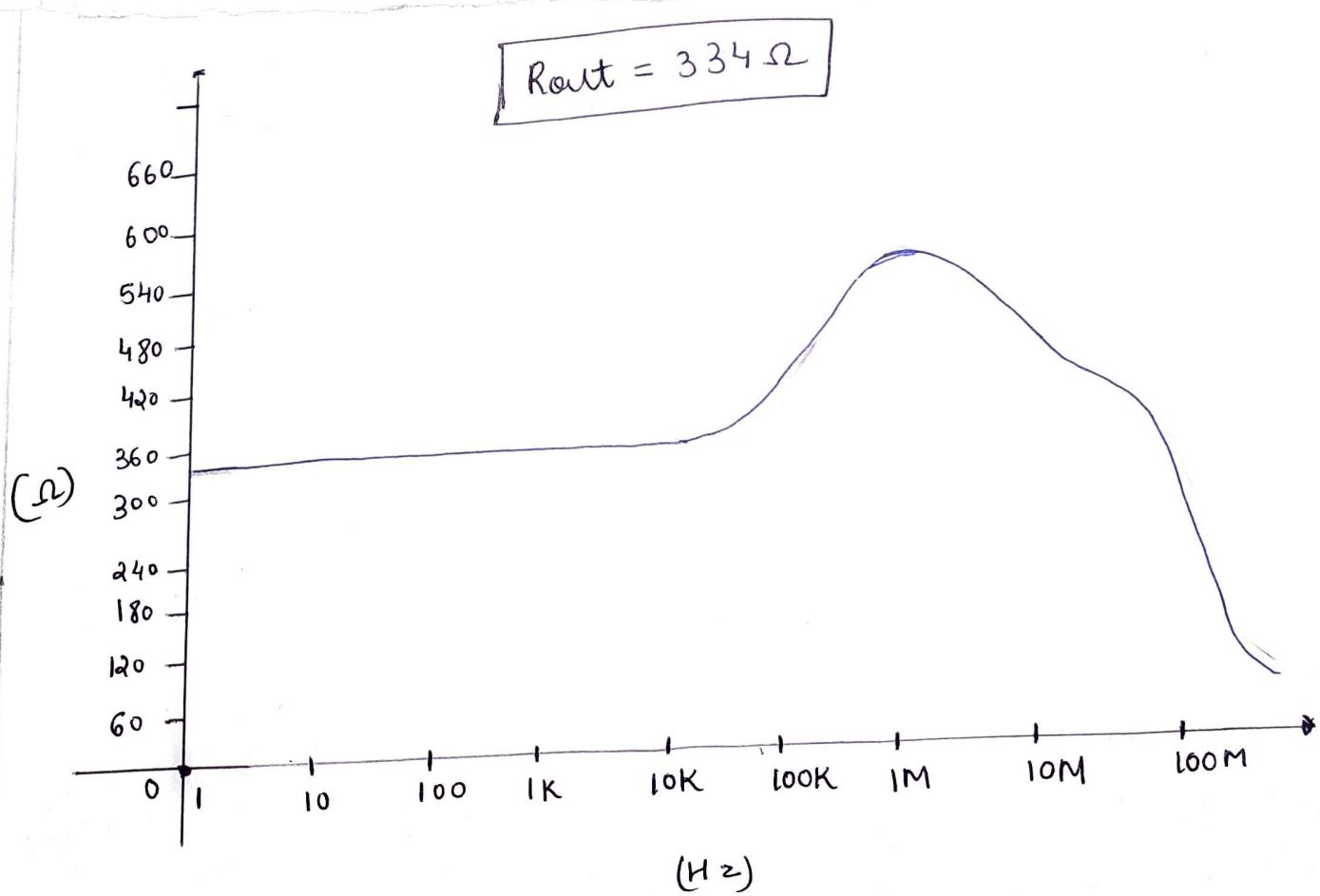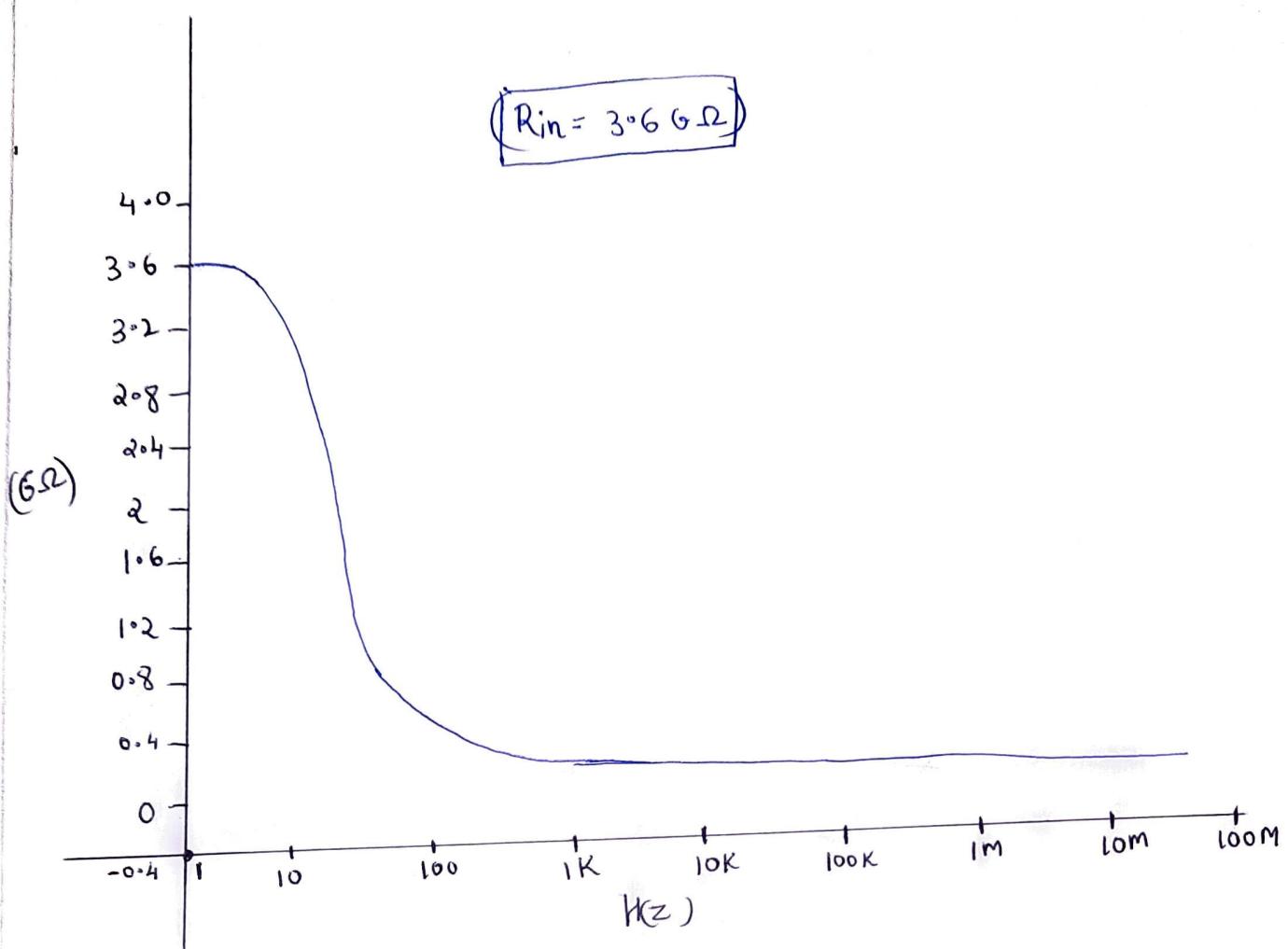

# Problem- 2

## Code

```
* C:\Users\devan\Documents\assnmnt files(2)\final_q2 - Copy.asc
Q1 Vcc N001 N002 0 4
Q2 Vcc N002 out 0 4
Q3 N003 N003 N005 0 4
I1 Vcc N003 50μ
Vin in 0 SINE(2.8 10m 1k) AC 10m
V1 Vcc 0 3.3
Q4 N005 N005 0 0 4
Q5 out N003 N004 0 4
Q6 N004 N005 0 0 4
C2 out 0 1p
Q9 out N003 N004 0 4
Q10 N004 N005 0 0 4
Q11 out N003 N004 0 4
Q12 N004 N005 0 0 4
R1 N001 in 40k
V2 out 0 1.71008
.model NPN NPN
.model PNP PNP
.lib C:\Users\devan\Documents\LTspiceXVII\lib\cmp\standard.bjt
.include mue1.txt
;dc vin 1.3 10 0.0001
;ac dec 1000 1 100Meg
.MODEL 1 ako:BC107A
.MODEL 2 ako:BC107B
.MODEL 3 ako:BC108A
.op
.plot Ie(Q2)/Ib(Q1)
.MODEL 4 ako:BC108B
* 1700
* 1.71057
.backanno
.end
```

## Error Log

```
Circuit: * C:\Users\devan\Documents\assnmnt files(2)\final_q2 - Copy.asc

Direct Newton iteration for .op point succeeded.
Semiconductor Device Operating Points:
      --- Bipolar Transistors ---
Name:      q12      q11      q10      q9      q8
Model:     4        4        4        4        4
```

Ib:	2.98e-07	2.94e-07	2.98e-07	2.94e-07	3.72e-16
Ic:	4.79e-05	4.76e-05	4.79e-05	4.76e-05	1.74e-09
Vbe:	5.86e-01	5.85e-01	5.86e-01	5.85e-01	3.17e-01
Vbc:	-8.67e-04	-5.38e-01	-8.67e-04	-5.38e-01	-1.33e+00
Vce:	5.86e-01	1.12e+00	5.86e-01	1.12e+00	1.65e+00
BetaDC:	1.61e+02	1.62e+02	1.61e+02	1.62e+02	4.67e+06
Gm:	1.85e-03	1.84e-03	1.85e-03	1.84e-03	5.97e-08
Rpi:	1.08e+05	1.10e+05	1.08e+05	1.10e+05	2.01e+08
Rx:	0.00e+00	0.00e+00	0.00e+00	0.00e+00	0.00e+00
Ro:	1.24e+06	1.26e+06	1.24e+06	1.26e+06	3.95e+10
Cbe:	1.98e-11	1.98e-11	1.98e-11	1.98e-11	1.49e-11
Cbc:	5.38e-12	4.38e-12	5.38e-12	4.38e-12	3.69e-12
Cjs:	0.00e+00	0.00e+00	0.00e+00	0.00e+00	0.00e+00
BetaAC:	2.01e+02	2.02e+02	2.01e+02	2.02e+02	1.20e+01
Cbx:	0.00e+00	0.00e+00	0.00e+00	0.00e+00	0.00e+00
Ft:	1.17e+07	1.21e+07	1.17e+07	1.21e+07	5.09e+02
Name:	q7	q6	q5	q4	q3
Model:	4	4	4	4	4
Ib:	3.72e-16	2.98e-07	2.94e-07	2.98e-07	3.02e-07
Ic:	1.74e-09	4.79e-05	4.76e-05	4.79e-05	4.88e-05
Vbe:	3.17e-01	5.86e-01	5.85e-01	5.86e-01	5.86e-01
Vbc:	-1.33e+00	-8.67e-04	-5.38e-01	0.00e+00	0.00e+00
Vce:	1.65e+00	5.86e-01	1.12e+00	5.86e-01	5.86e-01
BetaDC:	4.67e+06	1.61e+02	1.62e+02	1.61e+02	1.61e+02
Gm:	5.97e-08	1.85e-03	1.84e-03	1.85e-03	1.89e-03
Rpi:	2.01e+08	1.08e+05	1.10e+05	1.08e+05	1.07e+05
Rx:	0.00e+00	0.00e+00	0.00e+00	0.00e+00	0.00e+00
Ro:	3.95e+10	1.24e+06	1.26e+06	1.24e+06	1.22e+06
Cbe:	1.49e-11	1.98e-11	1.98e-11	1.98e-11	1.98e-11
Cbc:	3.69e-12	5.38e-12	4.38e-12	5.38e-12	5.38e-12
Cjs:	0.00e+00	0.00e+00	0.00e+00	0.00e+00	0.00e+00
BetaAC:	1.20e+01	2.01e+02	2.02e+02	2.01e+02	2.01e+02
Cbx:	0.00e+00	0.00e+00	0.00e+00	0.00e+00	0.00e+00
Ft:	5.09e+02	1.17e+07	1.21e+07	1.17e+07	1.19e+07
Name:	q2	q1			
Model:	4	4			
Ib:	7.15e-07	1.23e-08			
Ic:	1.42e-04	7.02e-07			
Vbe:	6.13e-01	4.76e-01			
Vbc:	-9.77e-01	-5.00e-01			
Vce:	1.59e+00	9.77e-01			
BetaDC:	1.99e+02	5.70e+01			
Gm:	5.49e-03	2.71e-05			
Rpi:	4.34e+04	2.92e+06			
Rx:	0.00e+00	0.00e+00			
Ro:	4.26e+05	8.56e+07			
Cbe:	2.18e-11	1.73e-11			
Cbc:	3.94e-12	4.43e-12			
Cjs:	0.00e+00	0.00e+00			
BetaAC:	2.39e+02	7.93e+01			
Cbx:	0.00e+00	0.00e+00			
Ft:	3.40e+07	1.99e+05			

Date: Sun Apr 11 22:38:02 2021

```
Total elapsed time: 0.160 seconds.

tnom = 27
temp = 27
method = trap
totiter = 17
traniter = 0
tranpoints = 0
accept = 0
rejected = 0
matrix size = 26
fillins = 2
solver = Normal
Matrix Compiler1: 1.88 KB object code size
Matrix Compiler2: 2.25 KB object code size
```